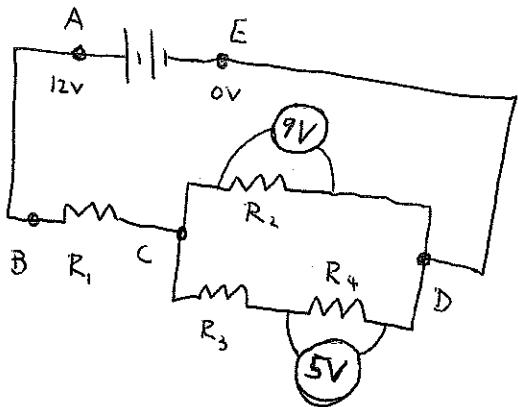


Circuit Intro:

①




a. Find ΔV_1 , ΔV_3 , ΔV_T

b. Find V_A, V_B, V_C, V_D, V_E

c. If $R_1 = 100\Omega$ Find R_{BD}


d. If $R_1 = 100\Omega$ and $R_3 = 400\Omega$ Find R_2 and R_4

2.

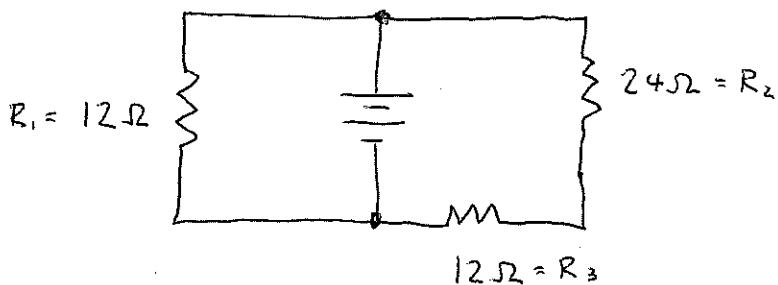

If $\Delta V_3 = 2.0\text{V}$ Find: ΔV_1 , ΔV_2 , ΔV_T , I_1, I_2, I_3 and I_T .

3.

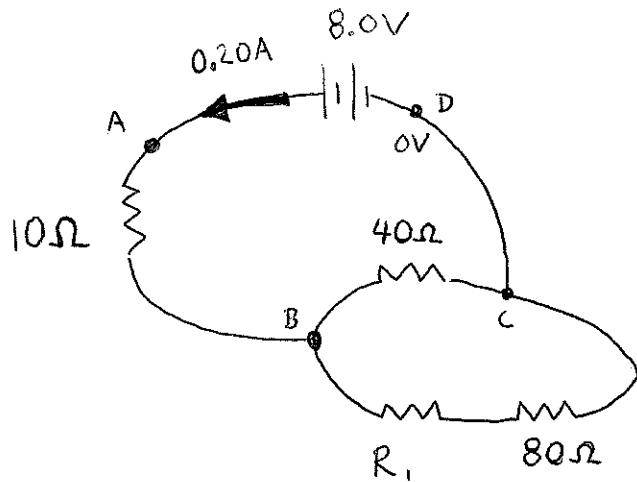a. Find V_A, V_B, V_C b. Find R_1

$$4. V_G = 0V$$

$$V_E = 12V$$

$$V_B = 8V$$


$$V_A = 2V$$

$$R_6 = 10\Omega$$

$$R_1 = 2\Omega$$

$$I_2 = 0.1A$$

$$R_3 = 80\Omega$$

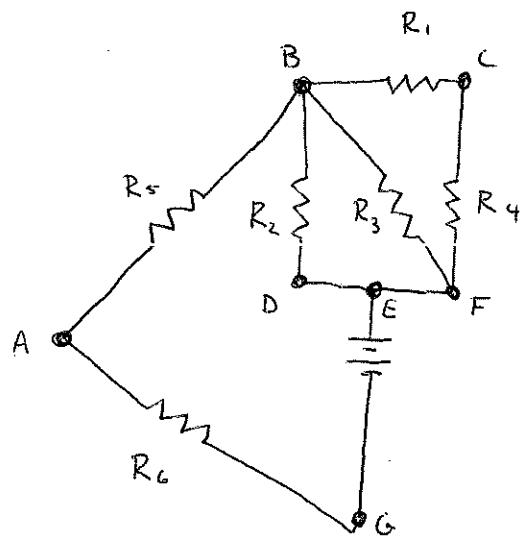Find R_2, R_4, R_5